



OSNOVE DIGITALNE ELEKTRONIKE

Minimizacija logičkih funkcija

Zdravko Kunić
zdravko.kunic@algebra.hr



Minimizacija logičkih funkcija

Ishod 4 Minimizirati i implementirati složene logičke funkcije uporabom osnovnih logičkih sklopova. Implementirati složene logičke funkcije uporabom složenih logičkih sklopova.


Sadržaj predavanja

- Minimum Booleove funkcije
- K tablice
- Minimizacija K tablicama

Booleova funkcija

- Booleova funkcija je opis digitalnog sklopa:
 - operator \Leftrightarrow osnovni logički sklop
 - izraz koji utvrđuje Booleovu funkciju \Leftrightarrow sklop
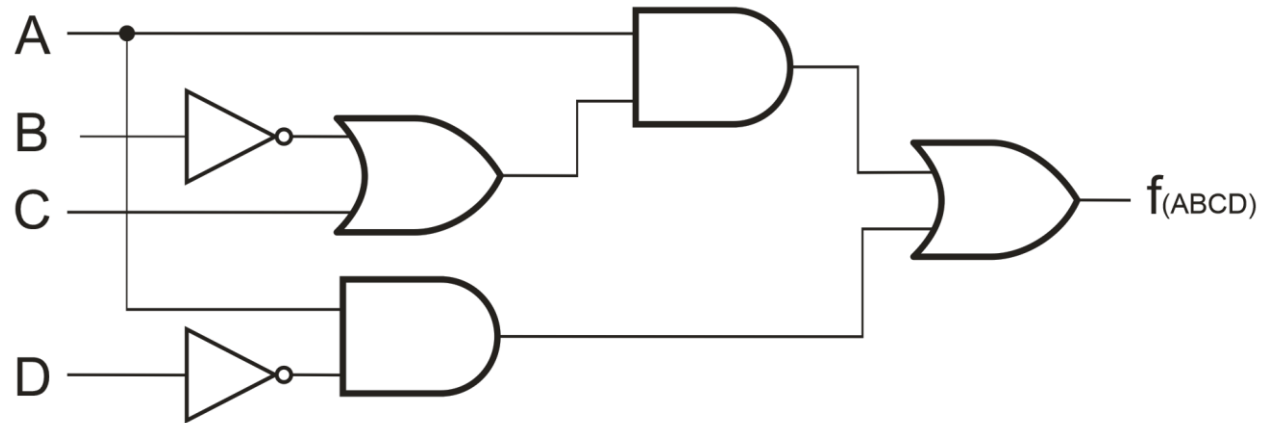
$$f = A(\overline{B} + C) + A\overline{D}$$



Minimizacija logičke funkcije

- Postupak svođenja funkcije na minimalan broj elemenata
- Određivanje izraza unutar velikog broja ekvivalentnih izraza, koji zadovoljava kriterije jednostavnosti
- Pronalaženje izraza koji minimizira odabranu **mjeru složenosti** za zadanu funkciju od n varijabli iz skupa mogućih funkcija:
 - Realizacija logičkog sklopa s najmanjim brojem elemenata, donosi:
 - Smanjenje cijene, potrošnje i veličine
 - Povećanje brzine i pouzdanosti
- Niti jedan postupak minimizacije ne vodi do jedinstvenog rješenja
 - Često je moguće dobiti više različitih izraza za istu funkciju, a svi imaju isti broj elemenata

Minimum Booleove funkcije

- Zapis logičke funkcije:
 - s najmanjim brojem **logičkih operatora**
 - s najmanjim brojem **ulaznih varijabli**
- Kontradiktorni kriteriji jednostavnosti (uobičajeno u inženjerskoj praksi):
 - **Najveća brzina rada sklopa**
 - **Najjeftinije ostvarenje**

Kriterij minimizacije:


Izraz u obliku sume produkata se smatra minimiziranim ako ne postoji:

- niti jedan drugi ekvivalentni izraz s manje produkata
- niti jedan drugi ekvivalentni izraz s istim brojem produkata, ali manjim brojem literala
 - Literal predstavlja varijablu (ili njezin komplement)

Nema sustavnog algebarskog postupka koji vodi do minimalnog izraza!

Minimizacija - primjer

$$f = A\bar{B} + AB + \bar{A}\bar{B}$$

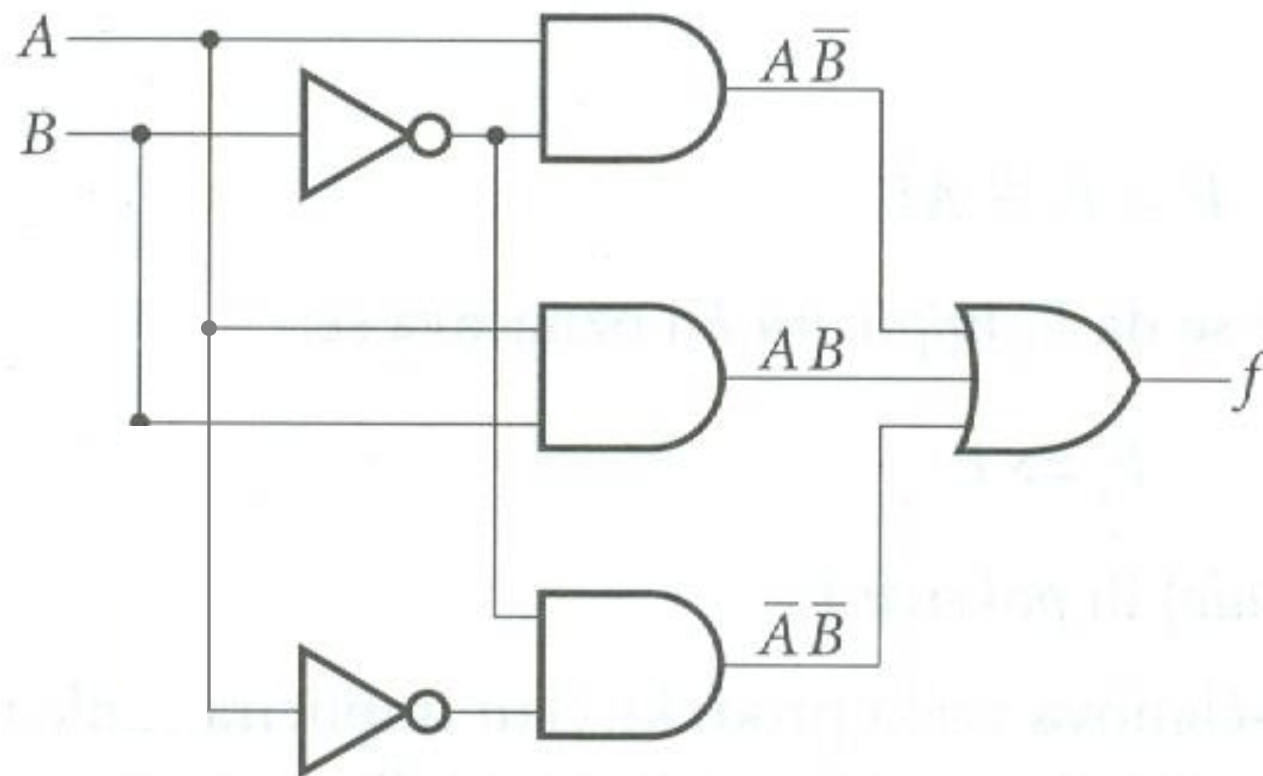


Minimizacija – rješenje 1:

$$\begin{aligned} f &= A\bar{B} + AB + \bar{A}\bar{B} \\ &= A(\bar{B} + B) + \bar{B}(A + \bar{A}) \\ &= A + \bar{B} \end{aligned}$$

Minimizacija – rješenje 2:
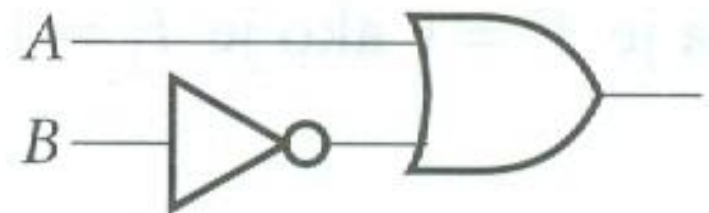
$$\begin{aligned} f &= A(\bar{B} + B) + \bar{A}\bar{B} \\ &= A + (\bar{A}\bar{B}) \\ &= (A + \bar{A})(A + \bar{B}) \\ &= A + \bar{B} \end{aligned}$$



K-tablice (Karnaughove tablice)

Grafički prikazi Booleovih funkcija u obliku 2D tablica

- **Polja** predstavljaju standardne članove (produkte/sume)
 - susjedna polja se razlikuju u samo jednoj varijabli! (kao kod Grayevog kôda)

A	B	f
0	0	α_0
0	1	α_1
1	0	α_2
1	1	α_3

f(A,B)		A	
		0	1
B	0	α_0	α_2
	1	α_1	α_3

K-tablice

- Grafičke strukture s 2^n polja za prikaz
- „Pravokutne koordinate”, Grayev kod ($d_{\min} = 1$)
- Minimizacija se svodi na "grupiranje" polja
 - temeljeno na ljudskoj sposobnosti raspoznavanja uzoraka (1 i 0)
- K-tablice za $n > 2$ varijable su simetrične oko jedne stranice
 - superpozicija
- Praktična primjena: $n \leq 6$

Izgradnja K- tablice

f(A,B)		A	
		0	1
B	0	0	2
	1	1	3

f(A,B,C)			AB		
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

f(A,B,C,D)				AB	
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

f(A,B,C,D)			AB			
			00	01	11	10
CD	00	0	4	12	8	
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	

$$13 = 1101 \equiv AB\bar{C}D$$

$$12 = 1100 \equiv AB\bar{C}\bar{D}$$

$$15 = 1111 \equiv ABCD$$

$$09 = 1001 \equiv A\bar{B}\bar{C}D$$

$$05 = 0101 \equiv \bar{A}B\bar{C}D$$

Izgradnja K- tablica

		A			
		00	01	11	10
C	AB				
C	0	0	2	6	4
	1	1	3	7	5

B

		A			
		00	01	11	10
CD	AB				
C	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

B

D

Minimizacija (suma minterma)

		A	
B	A		
	\bar{A}		1
B	A		1
	\bar{A}		

$$f = A\bar{B} + AB = A(B + \bar{B}) = A$$

		A	
B	A		
	\bar{A}	1	
B	A	1	
	\bar{A}		

$$f = \bar{A}B + AB = B(\bar{A} + A) = B$$

Zakon simplifikacije (T8)

Minimizacija (suma minterma)

		<u>A</u>	
B	A	$\bar{A}\bar{B}$	$A\bar{B}$
	B	$\bar{A}B$	AB

		<u>A</u>	
B	A		1
	B	1	1

		<u>A</u>	
B	A	m_0	
	B		M_0

$$f = A\bar{B} + AB + \bar{A}B = \bar{A}\bar{B} + A\bar{B} + AB + \bar{A}B = A(B + \bar{B}) + B(A + \bar{A}) = A + B$$

K-tablice s 3 varijable

Članovi s 2 susjedne jedinice:

		A			
		00	01	11	10
C	0		1	1	
	1	1			1
		B			

		A			
		00	01	11	10
C	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5
		B			

Susjedne
ćelije

K-tablice s 3 varijable

Članovi s 4 susjedne jedinice

		A			
		00	01	11	10
C	0	1	1	1	1
	1				

B

$$f = \overline{C}$$

		A			
		00	01	11	10
C	0		1	1	
	1		1	1	

B

$$f = B$$

		A			
		00	01	11	10
C	0			1	1
	1		1	1	1

B

$$f = A + BC$$

K-tablice s 4 varijable

Članovi s 2 susjedne jedinice

Članovi s 4 susjedne jedinice

Minimizirana funkcija:

$$f = \overline{A}C + B\overline{C}\overline{D}$$

CD \ AB	A			
	00	01	11	10
00		1	1	
01				
11	1	1		
10	1	1		

K-tablice s 4 varijable

		A			
		00	01	11	10
C	00		1	1	
	01		1	1	
	11		1	1	
	10		1	1	

B

D

Članovi s 8 susjednih jedinica
 $f = B$

		A			
		00	01	11	10
C	00		1		
	01				
	11	1			1
	10		1		

B

D

Susjednost krajnjih redaka i stupaca
 $f = \overline{A}B\overline{D} + \overline{B}CD$

Upis funkcije u K tablicu

- Funkcija u obliku **sume minterma**:

$$\sum m_i$$

1 za svaki m_i (ostalo su 0)

- Funkcija u obliku **produkta maksterma**:

$$\prod M_i$$

0 za svaki M_i (ostalo su 1)

Upis funkcije u K-tablicu


$$f(A, B, C, D) = \sum m(5, 6, 9, 10, 13, 14)$$

		A			
		00	01	11	10
C	00				
	01		1	1	1
	11				
	10		1	1	1
		B			
		D			


		A			
		00	01	11	10
C	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10
		B			
		D			

Primjer minimizacije pomoću K-tablice
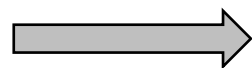
$$f(A, B, C, D) = \sum m(5, 6, 9, 10, 13, 14)$$



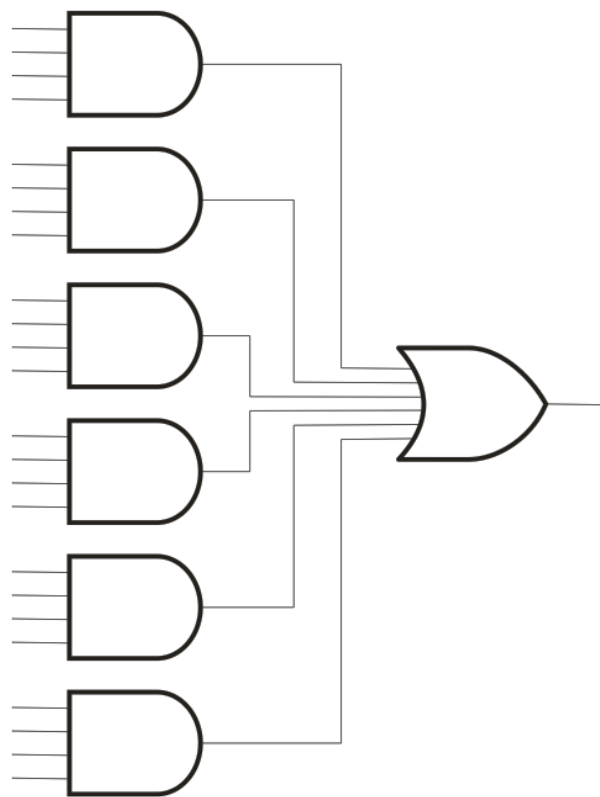
$$f(A, B, C, D) = B\bar{C}D + A\bar{C}D + BC\bar{D} + AC\bar{D}$$



		A			
		00	01	11	10
C	CD \ AB				
	00				
	01		1	1	1
	11				
	10		1	1	1

B

D

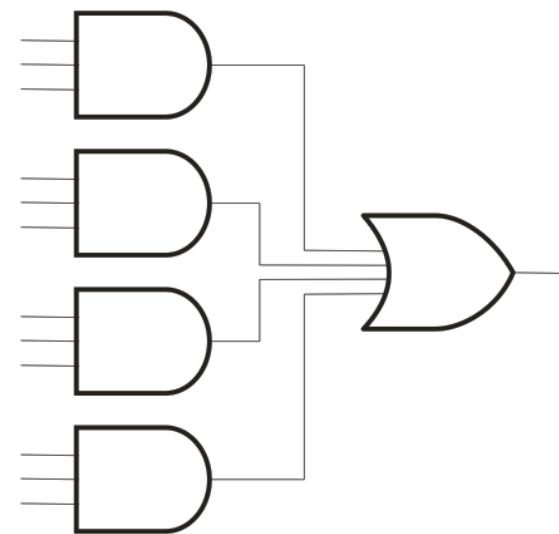

Minimizacija funkcije specificirane u obliku produkta maksterma:

$$f = \prod M(5,7,15)$$

- Postupak kao kod minterma, ali se zaokružuju 0
- Rezultat je produkt suma


$$f(A, B, C, D) = (A + \overline{B} + \overline{D}) \cdot (\overline{B} + \overline{C} + \overline{D})$$

		\overline{A}				
		00	01	11	10	
\overline{C}	00					\overline{D}
	01		0			
	11		0	0		
	10					
		\overline{B}				

Opća pravila grupiranja jedinica u K-tablici


- Grupiramo minterme (**1**) ako su u istom redu ili u istom stupcu
 - Ne grupiramo jedinice dijagonalno!
- Veličina grupe mora biti **potencija broja 2**
- Grupa mora biti **najveća moguća** (koristiti što manji broj grupa)
- Svi mintermi (**1**) moraju biti iskorišteni, čak i ako su samostalni
- Dozvoljeno je preklapanje grupa
- Dozvoljeno je omatanje grupa

Pravila grupiranja

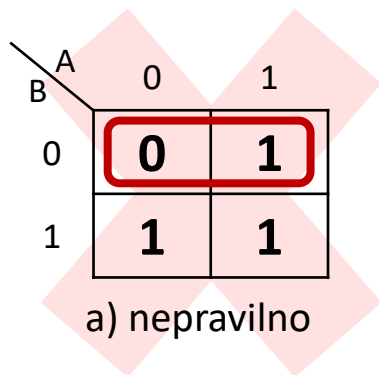

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the two cells in the top row (0 and 1). The entire diagram is crossed out with a large red 'X'.


a) **nepravilno**

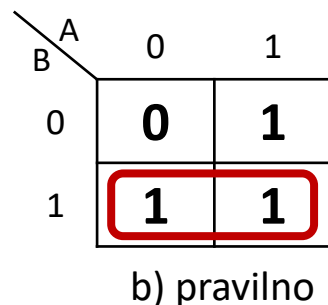

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the two cells in the bottom row (1 and 1). The entire diagram is not crossed out.


b) **pravilno**

a) Grupe sadrže samo jedinice

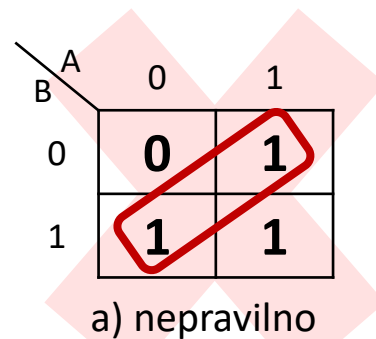

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red diagonal line groups the cells (0,1) and (1,1). The entire diagram is crossed out with a large red 'X'.


a) **nepravilno**

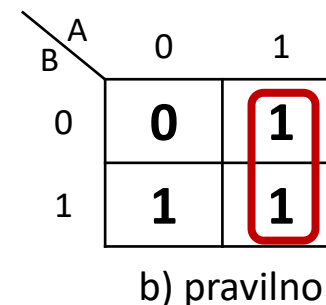

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the two cells in the right column (1 and 1). The entire diagram is not crossed out.


b) **pravilno**

b) Dijagonalne grupe nisu dozvoljene

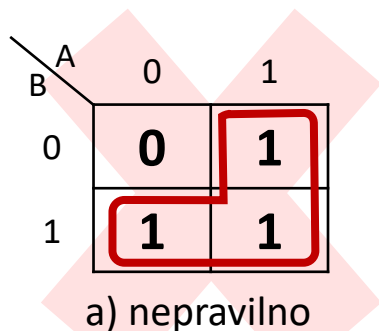

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the cells (0,1) and (1,1). The entire diagram is crossed out with a large red 'X'.


a) **nepravilno**

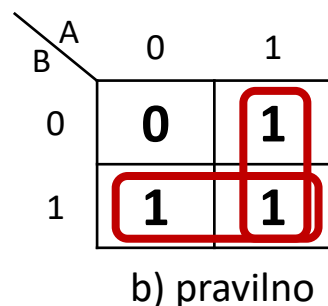

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the two cells in the right column (1 and 1). The entire diagram is not crossed out.


b) **pravilno**

c) Veličina grupe je potencija broja 2

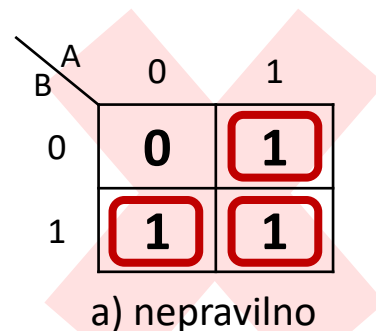

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. Two separate red rectangles group the cells (0,1) and (1,1) individually. The entire diagram is crossed out with a large red 'X'.

a) **nepravilno**

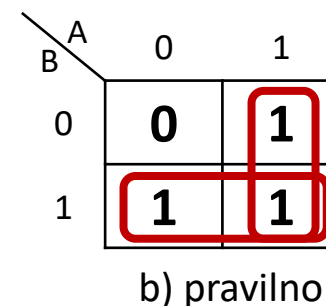

A 2x2 Karnaugh map with variables A and B. The top row (B=0) has values 0 and 1. The bottom row (B=1) has values 1 and 1. A red rectangle groups the two cells in the right column (1 and 1). The entire diagram is not crossed out.

b) **pravilno**

d) Grupe moraju biti najveće moguće

Nepotpuno specificirane funkcije

- Parcijalne funkcije
- Neke kombinacije argumenata se ne pojavljuju:
 - funkcijska vrijednost nije specificirana, X (engl. don't care)
 - X se interpretira onako kako najbolje odgovara pri minimizaciji (joker)!
- Pri postupku minimizacije je nužno pokriti sve **1**, ali ne i sve **X**
- X se interpretira kao 1 ($X = 1$) samo ako se time može proširiti zaokruženje
- Veće zaokruženje \sim jednostavniji Booleov izraz = jednostavniji sklop!

Primjer minimizacije nepotpuno specificirane funkcije

$$f = \sum m(2,5,15) + \sum d(0,1,3,4,7,9,13,14)$$

Bez minimizacije:

$$f(A, B, C, D) = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + ABCD$$

Minimizirano:

$$f(A, B, C, D) = \overline{A}\overline{B} + BD$$

		A			
		00	01	11	10
C	00	X	X		
	01	X	1	X	X
	11	X	X	1	
	10	1		X	
		B			


The background of the slide is a dense field of 3D question marks. Most are dark grey and recede into the background, while one large, bright orange question mark stands prominently in the center. The lighting creates highlights and shadows, giving the symbols a three-dimensional appearance.

Minimizacija logičkih funkcija




Zadatci za vježbu

Algebarski minimizirajte zadani sklop

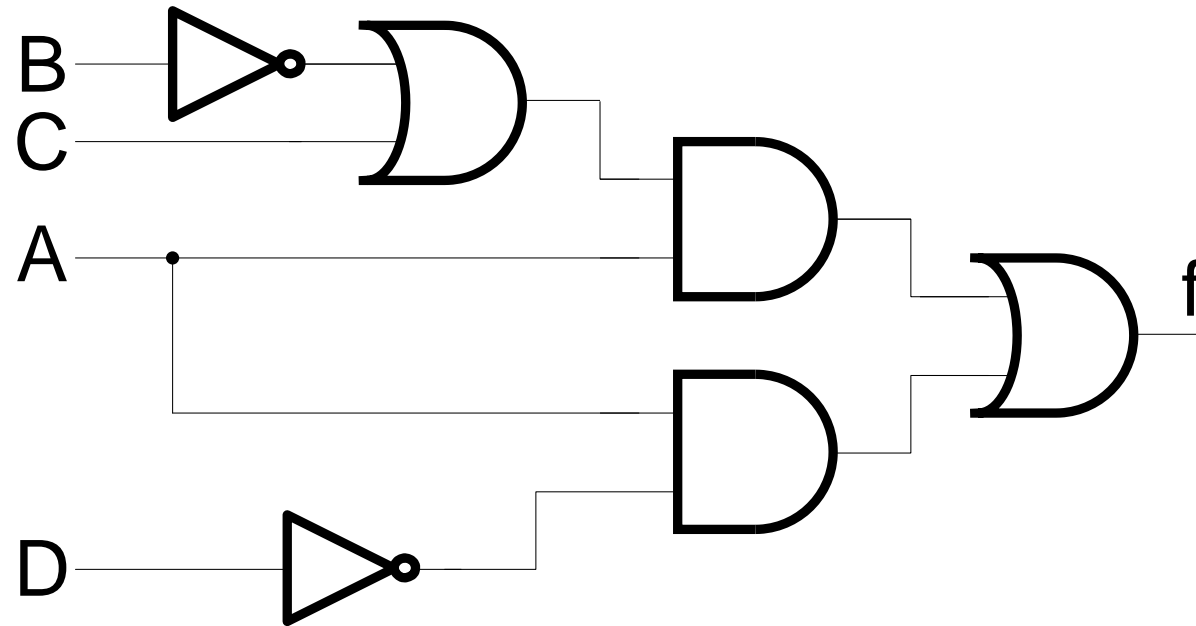

Rješenje

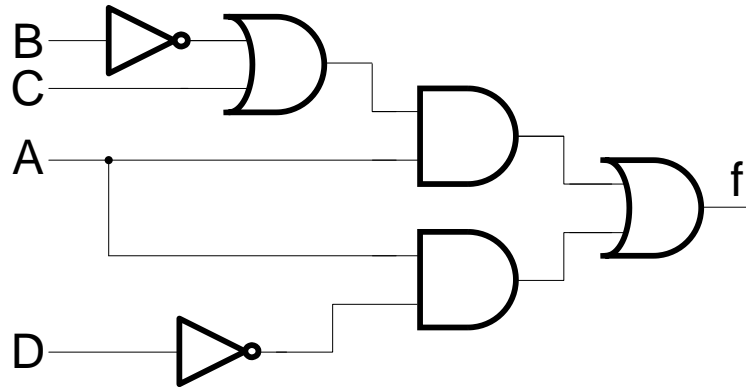

$$f = A(\overline{B} + C) + A\overline{D}$$

Supstitucija: $X = (\overline{B} + C)$; $Y = \overline{D}$

Aksiom 4.a: $AX + AY = A(X + Y)$

Supstitucija za X i Y : $= A[(\overline{B} + C) + \overline{D}]$

Aksiomi:


4. a) $A(B + C) = AB + AC$

b) $A + BC = (A + B)(A + C)$

Teorem:

5. a) $(A + B) + C = A + (B + C)$

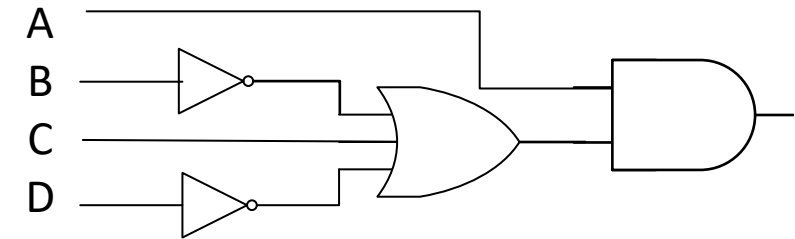b) $(A \cdot B) \cdot C = A \cdot (B \cdot C)$



$$f = A(\overline{B} + C + \overline{D})$$

Algebarska metoda minimizacije - primjer

$$\begin{aligned}f &= B\bar{C} + \bar{A}(\bar{A} + \bar{C})(B + C) \\&= B\bar{C} + \bar{A}(B + C) && \text{T.4.} \\&= B\bar{C} + \bar{A}B + \bar{A}C && \text{A.4.} \\&= B\bar{C} + \bar{A}B(C + \bar{C}) + \bar{A}C && \text{A1., A.4.} \\&= B\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + \bar{A}C && \text{A.4.} \\&= B\bar{C}(1 + \bar{A}) + \bar{A}C(B + 1) && \text{A.1., A.4.} \\&= B\bar{C} + \bar{A}C && \text{A.2., T.1.}\end{aligned}$$

Axioms:

1. a) $A + 0 = A$ b) $A \cdot 1 = A$

2. a) $A + \bar{A} = 1$ b) $A \cdot \bar{A} = 0$

Theorems:

1. a) $A + 1 = 1$ b) $A \cdot 0 = 0$

4. a) $A + AB = A$ b) $A \cdot (A + B) = A$

Projektirajte digitalni sklop za glasanje

Svaki član odbora od 3 člana ima prekidač za glasanje.


Prekidač ima dva položaja označena s DA i NE.

Prijedlog koji se stavi na glasanje je usvojen ako je za njega glasala većina članova.


- 1) Članove odbora označite s A, B i C.
- 2) Položajima prekidača DA i NE pridružite vrijednosti 0 i 1.
- 3) Usvojenom prijedlogu (oznaka y) pridijelite značenje 1.
- 4) Konstruirajte tablicu kombinacija.
- 5) Napišite logičku jednadžbu.
- 6) Minimizirajte sklop i nacrtajte ga.

Rješenje

A	B	C	y
0	0	0	
0	0	1	
0	1	0	
0	1	1	1
1	0	0	
1	0	1	1
1	1	0	1
1	1	1	1

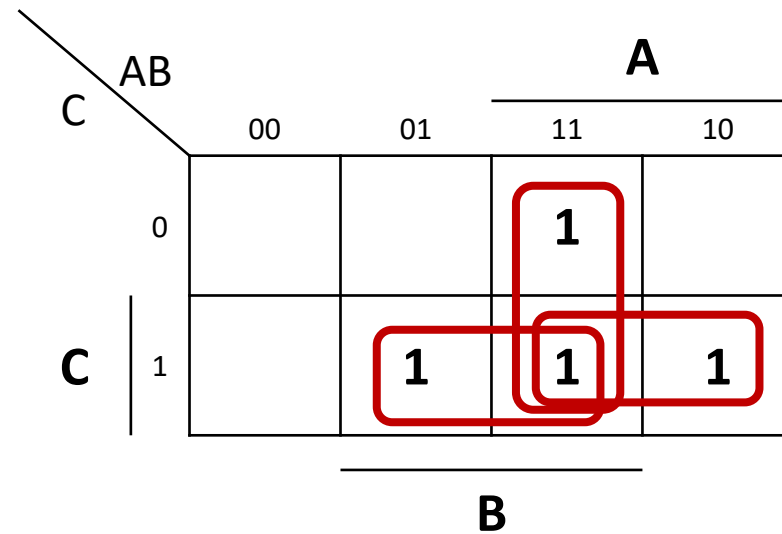
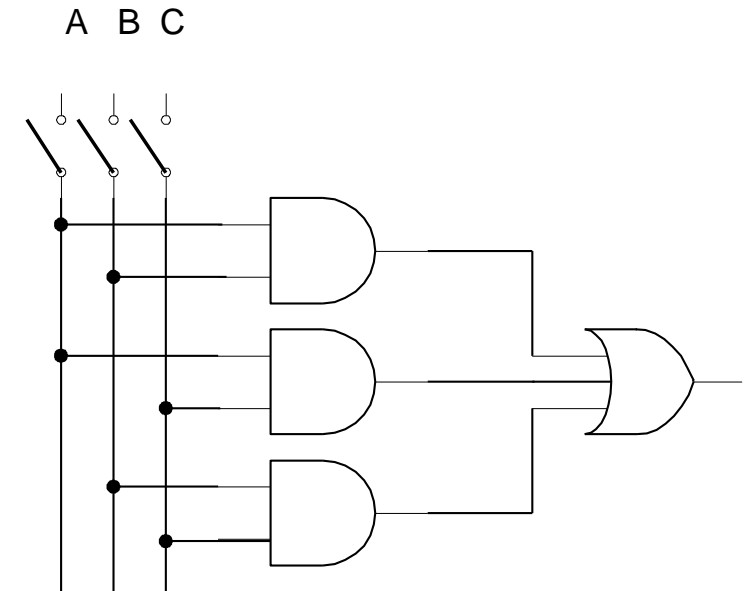
$$f = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$



$$f = AB + AC + BC$$


Zadatak

Projektirajte sklop za generiranje neparnog paritetnog bita za grupu od 3 binarne znamenke, A, B i C.

- 1) Nacrtajte blok shemu uređaja
- 2) Konstruirajte tablicu kombinacija
- 3) Minimizirajte
- 4) Napišite funkciju i nacrtajte sklop

Rješenje (1/2)

A	B	C	y
0	0	0	1
0	0	1	
0	1	0	
0	1	1	1
1	0	0	
1	0	1	1
1	1	0	1
1	1	1	

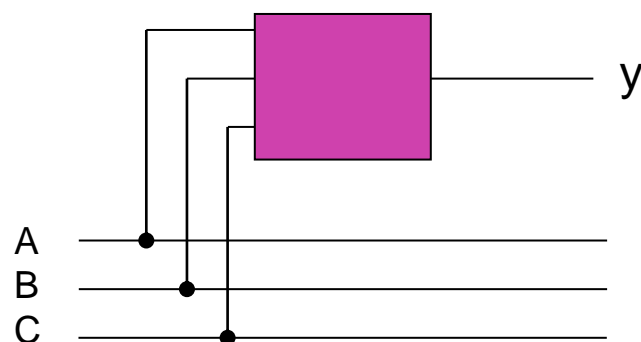

		A			
		00	01	11	10
C	0	1		1	
	1		1		1
		B			


Minimizacija K-tablicom nije moguća

$$f = \overline{A}BC + \overline{A}BC + A\overline{B}C + A\overline{B}C$$

Rješenje (2/2)

A	B	C	y
0	0	0	1
0	0	1	
0	1	0	
0	1	1	1
1	0	0	
1	0	1	1
1	1	0	1
1	1	1	
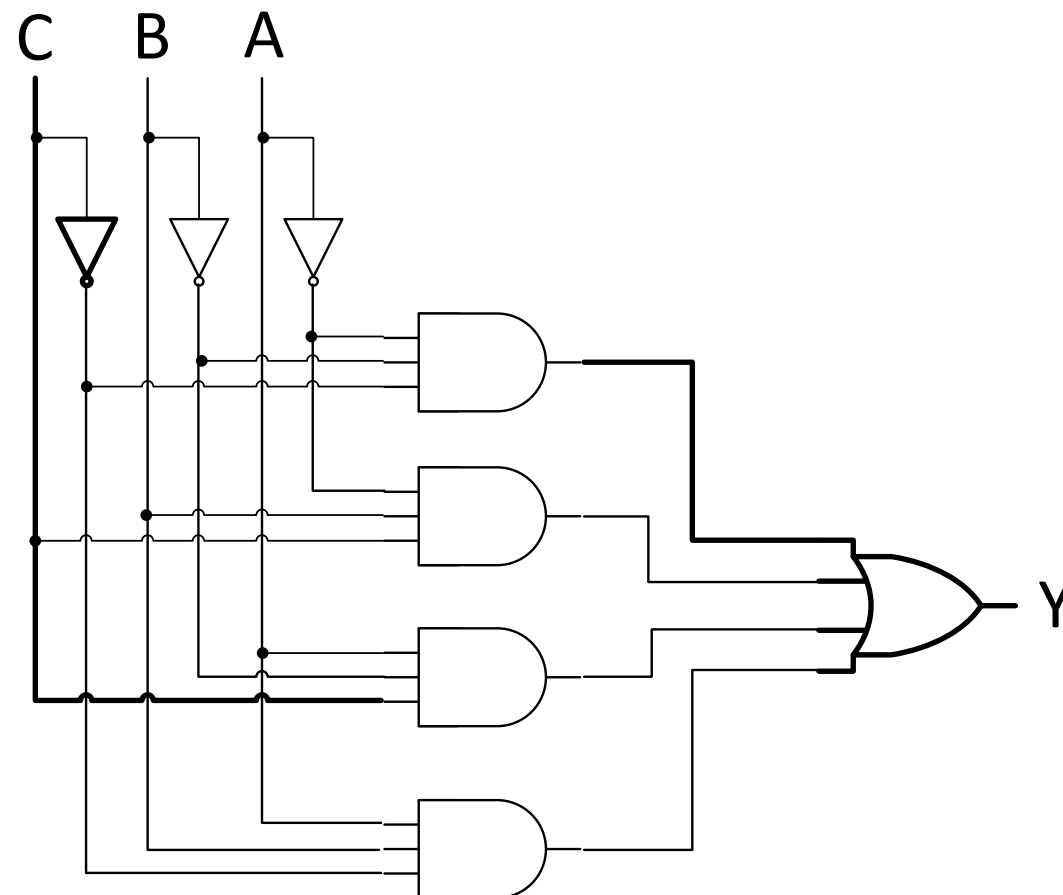
$$f = \overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}C + ABC\overline{C}$$



Minimizirajte funkciju

$$f(A, B, C) = \sum (1, 2, 5, 6, 7)$$

Rješenje

A	B	C	y
0	0	0	
0	0	1	1
0	1	0	1
0	1	1	
1	0	0	
1	0	1	1
1	1	0	1
1	1	1	1

$$y = f(A, B, C) = \sum (1, 2, 5, 6, 7)$$

		A			
		00	01	11	10
C	AB				
C	0		1	1	
	1	1		1	1

$$f = \overline{B}C + B\overline{C} + AC$$

Minimizirajte funkciju

$$f(A, B, C) = \sum (0, 2, 4, 6)$$

Rješenje

A	B	C	y
0	0	0	1
0	0	1	
0	1	0	1
0	1	1	
1	0	0	1
1	0	1	
1	1	0	1
1	1	1	

$$y = f(A, B, C) = \sum (0, 2, 4, 6)$$

		A			
		00	01	11	10
C	AB				
C	0	1	1	1	1
	1				
		B			

$$f = \bar{C}$$

Minimizirajte funkciju

$$f(A, B, C) = \prod (0, 2, 3, 7)$$

Rješenje

A	B	C	y
0	0	0	0
0	0	1	
0	1	0	0
0	1	1	0
1	0	0	
1	0	1	
1	1	0	
1	1	1	0

$$y = f(A, B, C) = \prod (0, 2, 3, 7)$$

		\overline{A}			
		00	01	11	10
\overline{C}	0	0	0		
	1		0	0	
		\overline{B}			

$$f = (A + C)(\overline{B} + \overline{C})$$


Minimizirajte funkciju

$$f(A, B, C) = \sum (0, 2, 3, 5, 7)$$

Rješenje

A	B	C	y
0	0	0	1
0	0	1	
0	1	0	1
0	1	1	1
1	0	0	
1	0	1	1
1	1	0	
1	1	1	1
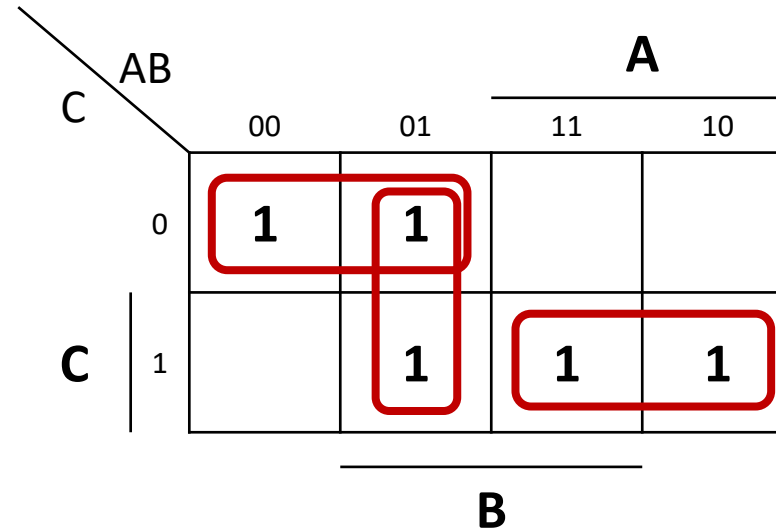
$$y = f(A, B, C) = \sum (0, 2, 3, 5, 7)$$





$$f = \overline{A} \overline{C} + \overline{A} B + AC$$

Primjeri zadataka s prethodnih ispita*

Ishod učenja 4 – 9 bodova - 25 min

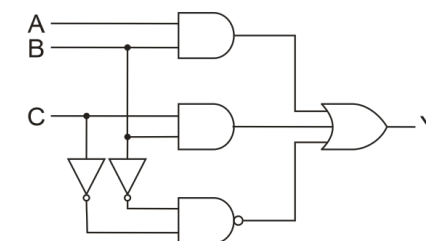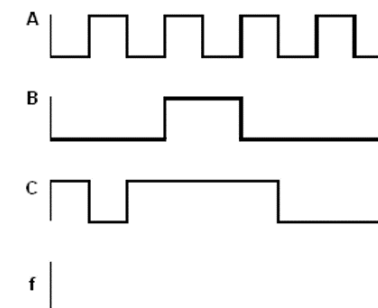1. **[I4_M / 2 boda]** Nacrtajte karakteristične simbole (u oba standarda) logičkog sklopa **ILI** s tri ulaza (0,5 bodova) i napišite tablicu kombinacija (0,5 bodova). Za zadani vremenski dijagram promjena ulaznih varijabli nacrtajte izlaznu funkciju (1 bod)
2. **[I4_M / 2 boda]** Za zadanu logičku shemu napišite logičku funkciju (1 bod) i tablicu kombinacija (1 bod)
3. **[I4_Ž / 3 boda]** Nacrtajte logičku shemu funkcije $f = (\overline{A}C + B)A\overline{B}$ ostvarene samo logičkim sklopovima I, ILI, NE (1 bod). Primjenom De Morganovih teorema transformirajte (1 bod) i nacrtajte (1 bod) izvedbu funkcije koja koristi samo **NI** logičke sklopove.
4. **[I4_Ž / 2 boda]** Pomoću K-tablice minimizirajte funkciju $f(A, B, C, D) = \sum(0, 1, 2, 4, 5, 6, 7, 13, 15)$. (1 bod za korektno ispunjenu tablicu, 1 bod za korektno napisanu potpuno minimiziranu funkciju)



* Primjer ispita je ilustrativan. Vrste zadataka na budućim brzim testovima i ispitima mogu biti drugačije.

LITERATURA:

- Uroš Peruško: Digitalni sustavi
 - Str. 129 - 147